

Experiment No: 02

Name of the Experiment: Design, Implementation, and performance Testing of an ~~ASK~~ ASK Digital Modulation circuit using IC-CD4016


Objectives:

- To design and implement an Amplitude Shift Keying (ASK) modulation circuit using the CD4016 IC.
- To analyze the working principle of ASK modulation and its significance in digital communication.
- To identify potential improvement for better performance.

Theory: ASK is a digital modulation technique in which the amplitude of the carrier signal varies based on the digital input signal.

- When the binary signal is '1' the carrier signal is transmitted.
- When the binary signal is '0', the carrier signal is suppressed.


Block diagram:

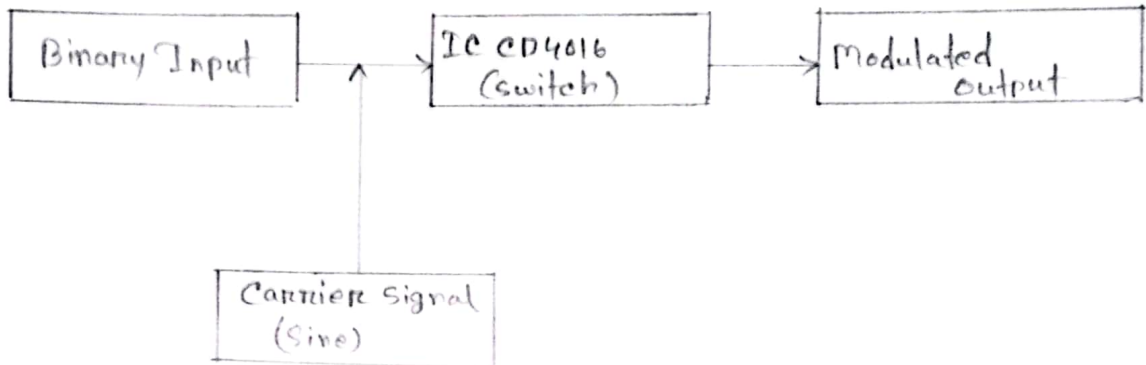

Apparatus Required:

- (1) IC CD4016
- (2) Oscilloscope
- (3) Function Generator
- (4) Power Supply
- (5) Bread Board
- (6) IC ~~7410~~ 74LS04
- (7) Connecting wires.

Working Diagram:

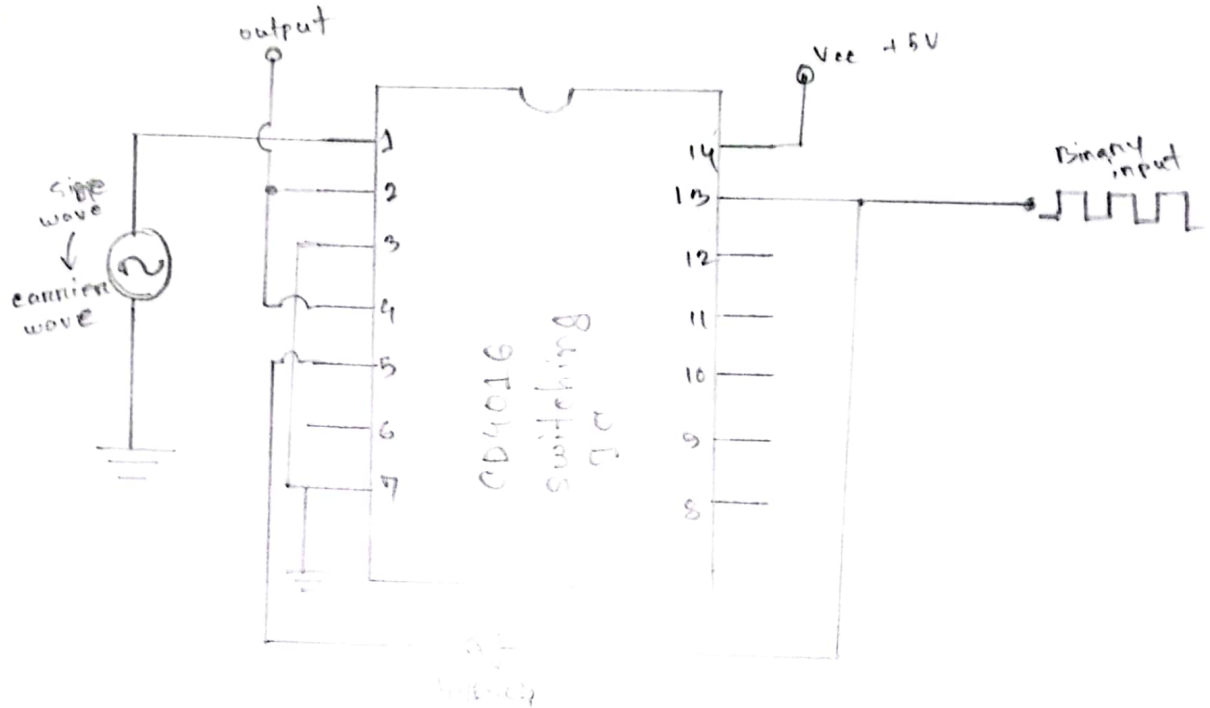

Procedures:

- (1) Connect the IC CD4016 on a breadboard.
- (2) Connect a function generator to provide a high-frequency sine wave as the carrier signal.
- (3) Provide a binary input using a function generator.
- (4) Connect the output to an oscilloscope for observation.
- (5) Power on the circuit.
- (6) Apply digital input and observe the ASK-modulated waveform.

Precautions:

- Ensure proper powersupply connections to prevent damage to IC chips.
- Avoid loose wiring to ensure signal transmission.
- Use an oscilloscope probe properly to avoid signal distortion.

Result: The oscilloscope display the ASK waveform, showing amplitude variations based on the input data.

Discussion:

we implement the circuit of ASK and by testing the performance we understand the operation of ASK digital modulation circuit.